

**DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY,
LONERE – RAIGAD -402 103
Mid Semester Examination – October - 2017**

Branch: M.Tech. (Electronics Engineering)

Sem.:- I

Subject with Subject Code:- VLSI System Design (MTEEC103)

Marks: 20

Date:-

Time:- 1 Hr.


Instructions:- Assume suitable data

(Marks)

Q.No.1 Attempt any one of the following (08)

a) Design layout of CMOS Inverter and explain the layout design rule.


ANS:

 

Design rule: Write color scheme and sizes of layer
Refer Example 2.5, page 87, Author: Wayne Wolf, Title: Modern VLSI Design, system on chip design.

b) What is structure of a Differential cascode Voltage switch logic (DCVSL)? Explain it and draw a schematic for two input AND/NAND gates in DCVSL.


ANS: Basic Principle of DCVSL

 

 (a) Basic principle


Refer -3.5.2 –DCVS Logic and Figure 3-29, page 147, 148

Author: Wayne Wolf, Title: Modern VLSI Design, system on chip design.



- Q.No. 2 Attempt any three of the following: (12)**
- a) What is meant by Pseudo NMOS Logic? Why use a Pseudo-NMOS Logic?**

ANS:

 

Refer -3.5.1 page 145 , Author:Wayne Wolf, Title: Modern VLSI Design ,system on chip design.

Or

Refer 2.5.4, Page 64, Author: Neil Weste, Title : CMOS VLSI Design

b) Assuming that $V_{gs}=3.3v$, $k'=73\mu A/v^2$, Compute the drain current through n-type transistors of the size $W/L=5/2$ at V_{ds} value of 2V.

ANS: Refer Example2.2, page 48 , Author:Wayne Wolf, Title: Modern VLSI Design ,system on chip design.

c) Define Noise margin. Explain low noise and high noise margin with Transfer characteristics of CMOS Inverter.

ANS: Refer 2.5.3, Page 62, Author: Neil Weste, Title : CMOS VLSI Design Or Refer -3.3.3 page 121 , Author:Wayne Wolf, Title: Modern VLSI Design ,system on chip design.

d) Describe following terms:

i) Wire and Vias

ii) Wire Parasitics

ANS: Refer:2.4, 2.4.1, page 62,65 , Author:Wayne Wolf, Title: Modern VLSI Design, system on chip design.