

Id	1
Question	Satellite Broadcasting in C band involves _____ uplink and _____ downlink frequency.
A	4 GHz and 6 GHz
B	6 GHz and 4 GHz
C	2.4 GHz and 5 GHz
D	None
--	
Marks	1.5
Unit	I

Id	2
Question	As the frequency increases the wavelength of the electromagnetic waves becomes
A	Larger
B	Smaller
C	Initially increases then decreases
D	Constant
--	
Marks	1.5
Unit	I

Id	3
Question	As frequency of electromagnetic becomes very high then
A	Component start to deviate from there electrical properties
B	Component starts to oscillate
C	Components will create unwanted noise in the output
D	None
--	
Marks	1.5
Unit	I

Id	4
Question	Why alternating current is preferred over direct current for transmission?
A	A.C. components are cheaper than D.C. Components
B	A.C. is more efficient than D.C.
C	A.C. has less losses than D.C.
D	Both b and c
--	
Marks	1.5
Unit	I

Id	5
Question	KCL and KVL Laws are suitable for....
A	Low frequency and D.C. circuits
B	High frequency circuits
C	Both a and b
D	None
--	
Marks	1.5
Unit	I

Id	6
Question	Intrinsic Impedance of air or free space (Z_0) is ____
A	377 Ω
B	37.7 Ω
C	3.77 Ω
D	None
--	
Marks	1.5
Unit	I

Id	7
Question	EM equations in positive z direction is given by $E_x = E_{0x} \cos(\omega t - \beta z)$ $H_y = H_{0y} \cos(\omega t - \beta z)$ Here E_{0x} and H_{0y} represents constant amplitude factors having units _____
A	Volts
B	V/m
C	Vm
D	V/A
--	
Marks	1.5
Unit	I

Id	8
Question	Intrinsic Impedance of the medium having relative permeability 1.5 and relative permittivity of 3.1 in Ohms is____
A	26.22
B	2.622
C	377
D	262.24
--	
Marks	1.5
Unit	I

Id	9
Question	In EM wave Electric field component and magnetic field components are _____
A	Mutually perpendicular to each other
B	Has phase difference of 90°
C	Transverse
D	All of the above
--	
Marks	1.5
Unit	I

Id	10
Question	Phase velocity of EM wave travelling in a medium having relative permeability 2 and relative permittivity 1.8
A	$3 \times 10^8 \text{m/s}$
B	$5 \times 10^8 \text{m/s}$
C	$1.58 \times 10^8 \text{m/s}$
D	$4 \times 10^8 \text{m/s}$
--	
Marks	1.5
Unit	I

Id	11
Question	Phase velocity of EM wave travelling in free space having frequency of 30MHz and 3GHz is.
A	$2.99 \times 10^8 \text{m/s}$ and $2.99 \times 10^8 \text{m/s}$
B	$4 \times 10^8 \text{m/s}$ and $5 \times 10^8 \text{m/s}$
C	$4 \times 10^8 \text{m/s}$ and $3.5 \times 10^8 \text{m/s}$
D	$2 \times 10^8 \text{m/s}$ and $5 \times 10^8 \text{m/s}$
--	
Marks	1.5
Unit	I

Id	12
Question	X Band has frequency range _____
A	8-12.5 GHz
B	2-4 GHz
C	2.4-8 GHz
D	4-6 GHz
--	
Marks	1.5
Unit	I

Id	13
Question	Capacitor with capacitance 1PF and inductor of 1nF at 60Hz has reactance values respectively.
A	$2.65 * 10^9 \Omega$ and $3.77 * 10^{-7} \Omega$
B	$3.77 * 10^{-7} \Omega$ and $2.65 * 10^9 \Omega$
C	$8.65 * 10^9 \Omega$ and $3.77 * 10^{-7} \Omega$
D	$3.77 * 10^9 \Omega$ and $8.65 * 10^{-7} \Omega$
--	
Marks	1.5
Unit	I

Id	14
Question	A cylindrical copper conductor of radius 0.5mm, length 80mm and conductivity of 64.516. Calculate its DC resistance
A	4.96 mΩ
B	8.15 mΩ
C	5.23 mΩ
D	1.58 mΩ
--	
Marks	1.5
Unit	I

Id	15
Question	As the frequency increases resistance at the center of the conductor_____
A	Decreases
B	Increases
C	Constant
D	None
--	
Marks	1.5
Unit	I

Id	16
Question	The skin effect is a phenomenon observed in
A	Insulators
B	Dielectrics
C	Conductors
D	Semiconductors
--	
Marks	1.5
Unit	I

Id	17
Question	Calculate the skin depth of a conductor in μm , having a conductivity of 200 units. The wave frequency is 10 GHz in air.
A	355.8
B	3.558
C	35.58
D	0.3558
--	
Marks	1.5
Unit	I

Id	18
Question	The relation between the skin depth and frequency is given by
A	Skin depth $\propto f$
B	Skin depth $\propto 1/f$
C	Skin depth $\propto \sqrt{f}$
D	Skin depth $\propto 1/\sqrt{f}$
--	
Marks	1.5
Unit	I

Id	19
Question	On what factors does the skin effect depend upon?
A	Cross section of the conductors.
B	Supply frequency.
C	Permeability of the conductor.
D	All of these
--	
Marks	1.5
Unit	I

Id	20
Question	What is the cause of skin effect?
A	Supply frequency.
B	Self inductance of conductor.
C	High sensitive material in the centre.
D	Both (a) and (b)
--	
Marks	1.5
Unit	I

Id	21
Question	The conductor carries more current on the surface in comparison to its core. What is this phenomenon called?
A	Ferranti effect.
B	Proximity effect.
C	Faraday's effect
D	Skin effect.
--	
Marks	1.5
Unit	I

Id	22
Question	Skin effect is negligible for what supply frequency and for what diameter?
A	< 50 Hz and < 1 cm.
B	< 50 Hz and > 1 cm.
C	> 50 Hz and < 1 cm.
D	> 50 Hz and > 1 cm.
--	
Marks	1.5
Unit	I


Id	23
Question	Which one of the following is not the type of High frequency Resistor?
A	Carbon composite resistor
B	Wire-wound resistor
C	Metal-film resistor
D	GaAs Resistor
--	
Marks	1.5
Unit	I

Id	24
Question	Determine the radius of AWG 26 wire
A	0.2032mm
B	0.4064mm
C	0.9872mm
D	0.6421mm
--	
Marks	1.5
Unit	I


Id	25
Question	Determine the diameter of AWG 32 wire
A	8 mils
B	6 mils
C	4 mils
D	5 mils
--	
Marks	1.5
Unit	I


Id	26
Question	Determine the diameter of AWG 50 wire
A	0.0254mm
B	0.0563mm
C	0.0872mm
D	0.0421mm
--	
Marks	1.5
Unit	I

Id	27
Question	Determine the radius of AWG 38 wire
A	8 mils
B	6 mils
C	4 mils
D	2 mils
--	
Marks	1.5
Unit	I

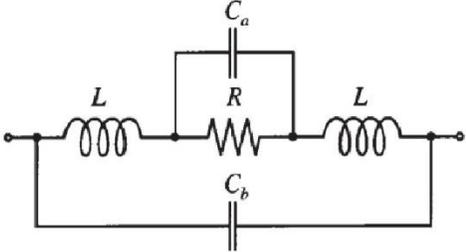Id	28
Question	<p>The below figure shows electric equivalent circuit representation of the resistor. What is the capacitance C_b?</p> <div style="text-align: center;">  <p>Electric equivalent circuit representation of the resistor.</p> </div>
A	Interlead capacitance
B	stray capacitance
C	coupling capacitance
D	None
--	
Marks	1.5
Unit	I

Id	29
Question	As the frequency increases, the stray capacitance becomes dominant, which causes the impedance of the resistor.....
A	Decrease
B	Increase
C	Upto resonance decreases and then increases
D	None
--	
Marks	1.5
Unit	I

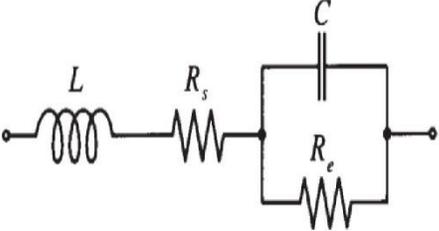Id	30
Question	<p>The below figure shows equivalent circuit of</p>  <p>The diagram shows an equivalent circuit. It starts with an inductor labeled L in series with a resistor labeled R_s. This series combination is connected to a parallel network. The parallel network consists of a capacitor labeled C and a resistor labeled R_e. The circuit ends with two terminals on the right.</p>
A	High Frequency Resistor
B	High Frequency Capacitor
C	High Frequency Inductor
D	None
--	
Marks	1.5
Unit	I

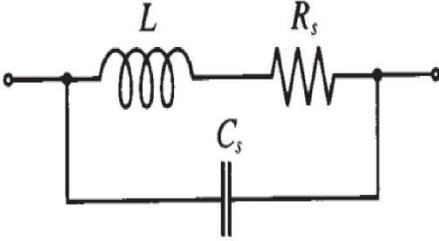Id	31
Question	<p>The below figure shows equivalent circuit of</p>  <p>The diagram shows an equivalent circuit with two terminals on the left and two terminals on the right. Between the left terminals, there is an inductor labeled L. Between the right terminals, there is a resistor labeled R_s. A capacitor labeled C_s is connected in parallel across both the inductor and the resistor.</p>
A	High Frequency Resistor
B	High Frequency Capacitor
C	High Frequency Inductor
D	None
--	
Marks	1.5
Unit	I

Id	32
Question	At low frequencies for ideal capacitor there is _____ between the two parallel plates.
A	No current flow
B	Less current flow
C	High current flow
D	Leakage current flow
--	
Marks	1.5
Unit	I

Id	33
Question	At high frequencies dielectric material become
A	Lossy
B	Insulator
C	Conductor
D	None
--	
Marks	1.5
Unit	I

Id	34
Question	At high frequencies, which parameter is significant?
A	Conduction current
B	Displacement current
C	Attenuation constant
D	Phase constant
--	
Marks	1.5
Unit	I

Id	35
Question	The loss tangent is also referred to as
A	Attenuation
B	Propagation
C	Dissipation factor
D	Polarization
--	
Marks	1.5
Unit	I

Id	36
Question	The loss tangent of a wave propagation with an intrinsic angle of 20 degree is
A	Tan 20
B	Tan 40
C	Tan 60
D	Tan 80
--	
Marks	1.5
Unit	I

Id	37
Question	The expression for the loss tangent is given by
A	$\sigma/\omega\varepsilon$
B	$\omega\varepsilon/\sigma$
C	σ/ω
D	ω/ε
--	
Marks	1.5
Unit	I

Id	38
Question	The equivalent series resistance (ESR) is given by
A	$\frac{\tan \Delta_s}{\omega c}$
B	$\frac{\omega c}{\tan \Delta_s}$
C	ωc
D	None
--	
Marks	1.5
Unit	I

Id	39
Question	As equivalent series resistance $ESR \rightarrow 0$, Value of Loss tangent $\tan \Delta_s$ becomes
A	∞
B	0
C	1
D	Insufficient data
--	
Marks	1.5
Unit	I

Id	40
Question	Find the loss angle in degrees when the loss tangent is 1.
A	0
B	45
C	30
D	90
--	
Marks	1.5
Unit	I

Id	41
Question	For a perfect dielectric, which parameter will be zero?
A	Conductivity
B	Frequency
C	Permittivity
D	Permeability
--	
Marks	1.5
Unit	I

Id	42
Question	Calculate the velocity of a wave with frequency $2 * 10^9$ rad/s and phase constant of $4 * 10^8$ units.
A	0.5
B	5
C	0.2
D	2
--	
Marks	1.5
Unit	I

Id	43
Question	The intrinsic impedance is the ratio of square root of
A	Permittivity to permeability
B	Permeability to permittivity
C	Phase constant to wavelength
D	Wavelength to phase constant
--	
Marks	1.5
Unit	I

Id	44
Question	The expression for phase constant is given by
A	Phase constant $\beta = \omega\mu\epsilon$
B	Phase constant $\omega = \mu\epsilon$
C	Phase constant $\beta = \omega\sqrt{(\mu\epsilon)}$
D	Phase constant $\beta = 1/\omega\mu\epsilon$
--	
Marks	1.5
Unit	I

Id	45
Question	Which of the following materials has highest electrical conductivity
A	Steel
B	Aluminium
C	Copper.
D	Silver.
--	
Marks	1.5
Unit	I

Id	46
Question	The meaning of capacitance Cs in high frequency inductor circuit is
A	Series capacitance
B	Parasitic Shunt capacitance
C	Stray capacitance
D	Small capacitance
--	
Marks	1.5
Unit	I

Id	47
Question	The series resistance R_s in high frequency inductor circuit is
A	Composite effect of distributed capacitance C_d and resistance R_d
B	Series capacitance
C	Lead inductance effect
D	None
--	
Marks	1.5
Unit	I

Id	48
Question	Estimate the inductance value of RFC formed by N=3.5 turns of AWG 36 copper wire on 0.1inch air core assume that length of the coil is 0.05 inch.
A	61.4nH
B	50.5nH
C	30.2nH
D	92.8nH
--	
Marks	1.5
Unit	I


Id	49
Question	The behaviour of RFC deviates from expected behaviour of ideal inductance at high frequencies. Which of the following correctly explains its behaviour.
A	Initially impedance increases and post resonance impedance decreases
B	Initially impedance decreases and post resonance impedance increases
C	Remains constant
D	Increases.
--	
Marks	1.5
Unit	I

Id	50
Question	The size of chip resistor with size code 0402 in Length by Width in mils is.
A	40,20
B	04,02
C	04,20
D	40,02
--	
Marks	1.5
Unit	I


Id	51
Question	The size of chip resistor with size code 1206 in Length by Width in mils is.
A	120,06
B	12,60
C	12,06
D	120,60
--	
Marks	1.5
Unit	I

Id	52
Question	The size of chip resistor with size code 1218 in Length by Width in mils is.
A	120,180
B	12,18
C	120,18
D	12,180
--	
Marks	1.5
Unit	I

Id	53
Question	The size of chip resistor with size code 0802 in Length by Width in mils is.
A	80,20
B	08,02
C	08,20
D	80,02
--	
Marks	1.5
Unit	I

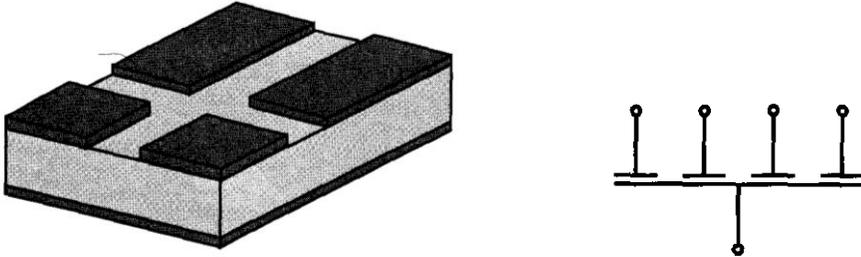Id	54
Question	<p>The figure shown below is ...</p> 
A	Quadrupole Chip Capacitor
B	Microstrip line
C	Electrolytic capacitor
D	Ceramic capacitor
--	
Marks	1.5
Unit	I

Id	55
Question	The size of single plate chip capacitor configuration for higher values of capacitance value will be
A	Lower
B	Higher
C	Constant
D	None
--	
Marks	1.5
Unit	I

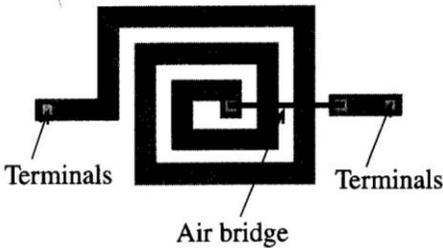Id	56
Question	<p>The following diagram shows construction of</p>  <p>The diagram shows a spiral inductor. It consists of a central square loop with four smaller square loops inside it, forming a spiral pattern. Two horizontal lines extend from the left and right sides of the spiral, labeled 'Terminals'. A small gap in the bottom horizontal line of the spiral is labeled 'Air bridge'.</p>
A	Flat coil configuration
B	Circular inductor
C	Terminal congfiguration
D	None
--	
Marks	1.5
Unit	I

Id	57
Question	Flat Coils are used in...
A	Integrated circuits
B	Hybrid circuits
C	Both a and b
D	None
--	
Marks	1.5
Unit	I

Id	58
Question	the order of the denominator polynomial obtained in transfer function is equal to (natural frequencies
A	Significant zeros
B	Poles and zeros
C	Zeros
D	the number of poles
--	
Marks	1.5
Unit	II

Id	59
Question	Number of poles in the transfer function indicates
A	Number of energy storing elements
B	Number of zeros
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	60
Question	The method of open-circuit time constants (OC's), also known as
A	Close circuit
B	Short circuit
C	zero value time constants
D	Both a and b
--	
Marks	1.5
Unit	II

Id	61
Question	all-pole transfer functions has
A	All poles
B	No zeros
C	Both a and b
D	No poles
--	
Marks	1.5
Unit	II

Id	62
Question	By equating the denominator of transfer function to zero, which among the following will be obtained?
A	Poles
B	Zeros
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	63
Question	Basically, poles of transfer function are the laplace transform variable values which causes the transfer function to become _____
A	Zero
B	Unity
C	Infinite
D	Average Value
--	
Marks	1.5
Unit	II

Id	64
Question	The SI unit for bandwidth is?
A	Hz
B	Watt
C	KHz
D	KW
--	
Marks	1.5
Unit	II

Id	65
Question	At bandwidth frequency range, the value of the current I is?
A	$\frac{I_m}{2}$
B	$\frac{I_m}{\sqrt{2}}$
C	I_m^2
D	I_m
--	
Marks	1.5
Unit	II

Id	66
Question	Bandwidth is the difference of _____ frequencies.
A	half power
B	Full power
C	Watt power
D	Double power
--	
Marks	1.5
Unit	II

Id	67
Question	For a sharp resonance, bandwidth is _____
A	Zero
B	High
C	Low
D	Infinity
--	
Marks	1.5
Unit	II

Id	68
Question	Q is a measure of _____
A	Resonance
B	Bandwidth
C	Selectivity
D	Either Resonance or Bandwidth
--	
Marks	1.5
Unit	II

Id	69
Question	<p>Given the polynomial as follows in Open circuit time constant method the coefficient b_n in the denominator polynomial is ...</p> $\frac{V_o(s)}{V_i(s)} = \frac{a_o}{(\tau_1 s + 1)(\tau_2 s + 1) \dots (\tau_n s + 1)}$
A	The product of all of the time constants
B	The sum of all of the time constants.
C	The average of all time constants
D	The geometric mean of all time constants
--	
Marks	1.5
Unit	II

Id	70
Question	<p>Given the polynomial as follows in Open circuit time constant method the coefficient b_1 in the denominator polynomial is ...</p> $\frac{V_o(s)}{V_i(s)} = \frac{a_o}{(\tau_1s + 1)(\tau_2s + 1)\dots(\tau_ns + 1)}$
A	The product of all of the time constants
B	The sum of all of the time constants.
C	The average of all time constants
D	The geometric mean of all time constants
--	
Marks	1.5
Unit	II

Id	71
Question	In Open circuit time constant method we normally_____
A	Neglect higher order terms
B	Neglect lower order terms
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	72
Question	The linear combination of these individual, local limitations yields an estimate of the total bandwidth is the statement of
A	Open circuit time constant method
B	Short circuit time constant method
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	73
Question	<p>In the below equation of open circuit time constant method R_{j0} is</p> $\omega_{h, est} = \frac{1}{m \sum_{j=1} R_{j0} C_j}$
A	Parallel resistance
B	Open circuit resistant facing jth capacitor
C	Short circuit resistance
D	None
--	
Marks	1.5
Unit	II

Id	74
Question	Open circuit time constant method estimate will be quite accurate if.....
A	System has Lower order poles
B	System has Less number of poles
C	A network has more number of higher order poles
D	A network of higher order happens to be dominated by one pole
--	
Marks	1.5
Unit	II

Id	75
Question	the true bandwidth of a two-pole system does depend on_____
A	Real part
B	Imaginary parts
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	76
Question	For two pole transfer function given below estimate of bandwidth value most accurate results are obtained for $\omega_h = \omega_n [1 - 2\zeta^2 + \sqrt{2 - 4\zeta^2 + 4\zeta^4}]^{0.5}$
A	$\zeta = 0.1$
B	$\zeta = 0.2$
C	$\zeta = 0.35$
D	$\zeta = 1$
--	
Marks	1.5
Unit	II

Id	77
Question	In Open circuit time constant method the coefficient b_1 neglects
A	Real part
B	Imaginary parts
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	78
Question	Open circuit time constants are concerned only with those capacitors that limit_____
A	High-frequency gain
B	Low-frequency gain
C	Both a and b
D	Mid-frequency gain
--	
Marks	1.5
Unit	II

Id	79
Question	The number of open-circuit time constants and the number of poles are_____
A	Equal
B	Not Equal
C	May be equal or not equal
D	Time constants > number of poles
--	
Marks	1.5
Unit	II

Id	80
Question	In a circuit if total capacitors are 4 and 1 inductor and 2 capacitors are parallel to each other then what are the number of time constants.
A	4
B	3
C	2
D	5
--	
Marks	1.5
Unit	II

Id	81
Question	The ratio of current from the dependent current source to the voltage between the left terminal and ground is _____
A	Transconductance
B	Effective transconductance
C	Conductance
D	Impedance
--	
Marks	1.5
Unit	II

Id	82
Question	Open circuit time constant method assumes ...
A	All pole transfer function
B	All zero transfer function
C	All pass transfer function
D	None
--	
Marks	1.5
Unit	II

Id	83
Question	Open circuit time constant method gives more accurate results when.....
A	All poles are conjugate
B	All poles are imaginary
C	All poles are complex
D	All poles are real
--	
Marks	1.5
Unit	II

Id	84
Question	Short-circuit time constant method works on the assumption that.....
A	All zeros exists
B	All poles exists
C	All of the zeros are at the origin, and that there are as many poles as zeros
D	Conjugate poles exists
--	
Marks	1.5
Unit	II

Id	85
Question	Short-circuit time constant method coefficient b_1 is
A	the product of all of the pole frequencies
B	the sum of all of the pole frequencies
C	the average of all of the pole frequencies
D	the geometric mean of all of the pole frequencies
--	
Marks	1.5
Unit	II

Id	86
Question	Short-circuit time constant method τ_{sc} is
A	the product of all of the pole frequencies
B	the sum of all of the pole frequencies
C	the average of all of the pole frequencies
D	the geometric mean of all of the pole frequencies
--	
Marks	1.5
Unit	II

Id	87
Question	The frequency calculated by Short-circuit time constant method is _____ than actual cutoff frequency
A	More
B	Less
C	Equal
D	May be more or less
--	
Marks	1.5
Unit	II

Id	88
Question	Short-circuit time constant method equation as shown the resistance R_{js} $\omega_{l, est} = \sum_{j=1}^m \frac{1}{R_{js} C_j}$
A	Parallel resistance
B	effective resistance facing each j^{th} capacitor with all of the other capacitors short-circuited
C	Open circuit resistant facing j^{th} capacitor
D	None
--	
Marks	1.5
Unit	II

Id	89
Question	the short circuit time constant estimate will be quite accurate if
A	A network of higher order happens to be dominated by one zero
B	A network of higher order happens to be dominated by one pole
C	A network has conjugate poles
D	None
--	
Marks	1.5
Unit	II

Id	90
Question	One must apply SC τ 's only to models that are appropriate to the _____ regime
A	High- Frequency
B	low-frequency
C	Mid-frequency
D	Both a and b
--	
Marks	1.5
Unit	II

Id	91	
Question	One must apply $OC\tau$'s only to models that are appropriate to the _____ regime	
A	High- Frequency	
B	low-frequency	
C	Mid-frequency	
D	Both a and b	
--		
Marks	1.5	
Unit	II	

Id	92
Question	In short circuit time constant method we normally_____
A	Neglect higher order terms
B	Neglect lower order terms
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	93
Question	<p>The time system takes for the impulse response to reach its “center of mass,” that is, the normalized value of its first moment.</p> $T_D \equiv \frac{\int_{-\infty}^{\infty} th(t)dt}{\int_{-\infty}^{\infty} h(t)dt}$
A	Time Delay
B	Delay of system connected in cascade form
C	Roll off time
D	None
--	
Marks	1.5
Unit	II

Id	94
Question	Rise time can be approximately given by
A	$2.2RC$
B	$2.2/RC$
C	$RC/2$
D	RC
--	
Marks	1.5
Unit	II

Id	95
Question	Compute the rise time of low pass filter having $R=1K\Omega$, $C=1\mu F$
A	2.2s
B	22ms
C	2.2ms
D	2200s
--	
Marks	1.5
Unit	II

Id	96
Question	The relation between Open-Circuit Time Constants, Risetime and Bandwidth is...
A	$BW \cong \frac{0.833}{\tau\sqrt{N}}$
B	$BW \cong \frac{\tau\sqrt{N}}{0.833}$
C	$BW \cong 0.833 * \tau\sqrt{N}$
D	$BW \cong \frac{1}{0.833 * \tau\sqrt{N}}$
--	
Marks	1.5
Unit	II

Id	97
Question	Which capacitors assists in preventing the loss of gain due to negative feedback without affecting the DC stability of R-C Coupled amplifier?
A	Coupling capacitors (C_c)
B	Bypass capacitors (C_E)
C	Both a and b
D	None
--	
Marks	1.5
Unit	II


Id	98
Question	Which among the following is not an advantage of RC coupled amplifiers?
A	High fidelity
B	No core distortion
C	No impedance matching
D	Wide frequency response
--	
Marks	1.5
Unit	II

Id	99
Question	Which among the below mentioned circuits resemble its behaviour similar to that of an amplifier in high frequency region, as the response decreases with an increase in frequency?
A	Simple high pass circuit
B	Simple low pass circuit
C	Simple bandpass circuit
D	Simple bandstop circuit
--	
Marks	1.5
Unit	II

Id	100
Question	Fidelity is nothing but an ability of amplifier to reproduce _____
A	Input signal without any distortion
B	Output signal without any distortion
C	Phase shift signal
D	Amplitude shift signal
--	
Marks	1.5
Unit	II

Id	101
Question	The value of dBm in power measurement is estimated by assuming the reference ,which is equal to.... _____
A	1mW
B	10mW
C	1/10 mW
D	1/100 mW
--	
Marks	1.5
Unit	II

Id	102
Question	Which region/s in frequency response curve of an amplifier maintains the constant level of gain and output voltage?
A	Low Frequency Region
B	Mid Frequency Region
C	High Frequency Region
D	None
--	
Marks	1.5
Unit	II




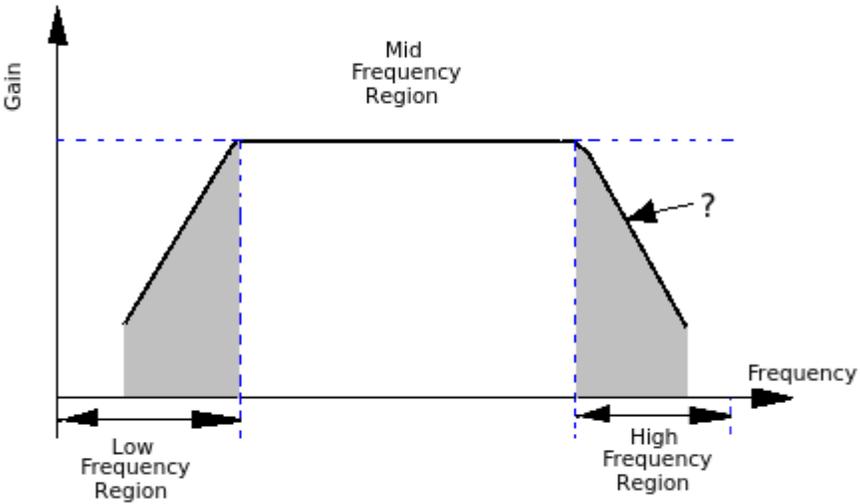
Id	103
Question	<p>What does an arrow indicate in the below drawn schematic for frequency response curve of RC coupled amplifier?</p> 
A	Ideal Frequency Response
B	Practical Frequency Response
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	104
Question	Voltage shunt feedback amplifier forms
A	A negative feedback
B	A positive feedback
C	Both positive and negative
D	None
--	
Marks	1.5
Unit	II

Id	105
Question	The value of feedback resistor and resistor connected in series with the input signal source are equal to $10\text{k}\Omega$ and $3.3\text{k}\Omega$. Calculate the closed loop voltage gain?
A	-6.7
B	-33
C	-13.3
D	-3.33
--	
Marks	1.5
Unit	II

Id	106
Question	The formula for closed loop voltage gain of inverting amplifier with feedback using open loop voltage gain and gain of feedback circuit is.(A is open loop gain)
A	$A_F = A/(1+AB)$
B	$A_F = -A/(1+AB)$
C	$A_F = -B/(1+AB)$
D	None
--	
Marks	1.5
Unit	II

Id	107
Question	Voltage shunt feedback amplifiers are also called as
A	Non-inverting amplifier with feedback
B	Non-inverting amplifier without feedback
C	inverting amplifier with feedback
D	inverting amplifier without feedback
--	
Marks	1.5
Unit	II

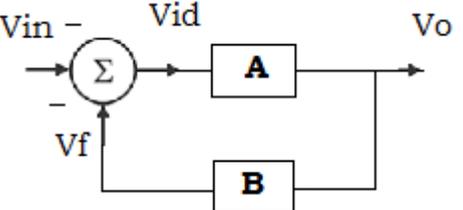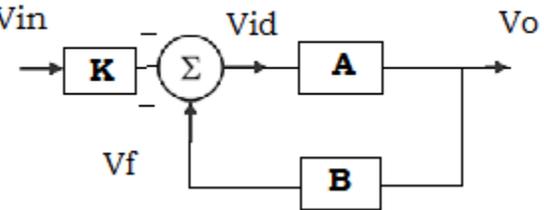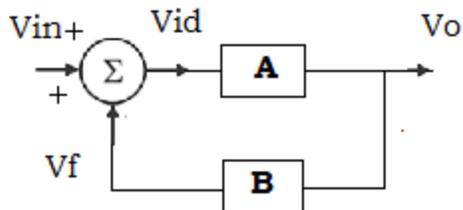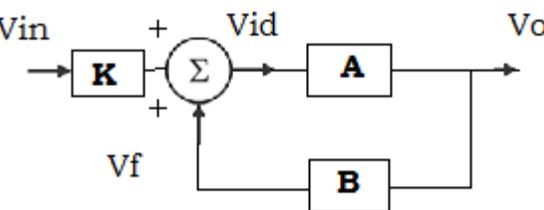Id	108
Question	Find the block diagram representation for inverting amplifier with feedback
A	
B	
C	
D	
--	
Marks	1.5
Unit	II

Id	109
Question	The inverting input inverting of the voltage shunt feedback resistor is a commonly named as
A	Terminal ground
B	Virtual ground
C	Virtual input
D	Resistive input
--	
Marks	1.5
Unit	II

Id	110
Question	How the peaking response is obtained?
A	Using a series LC network with op-amp
B	Using a series RC network with op-amp
C	Using a parallel LC network with op-amp
D	Using a parallel RC network with op-amp
--	
Marks	1.5
Unit	II

Id	111
Question	Open circuit time constants can grossly underestimate bandwidth if there arein the passband
A	Poles
B	Zeros
C	Both a and b
D	None
--	
Marks	1.5
Unit	II

Id	112
Question	A technique that satisfies large bandwidth at low cost is known as....
A	Biasing
B	Shunting
C	Shunt peaking.
D	None
--	
Marks	1.5
Unit	II

Id	113
Question	Shunt peaked amplifier is common-source configuration with addition of
A	Inductance
B	Capacitance
C	Resistancce
D	Conductance
--	
Marks	1.5
Unit	II

Id	114
Question	In shunt peaked amplifier if transistor is ideal then element controls bandwidth
A	Resistance (R)
B	Inductor (L)
C	Capacitance (C)
D	All of the above
--	
Marks	1.5
Unit	II

Id	115
Question	In shunt peaked amplifier loading on the output node represented by...
A	Resistance (R)
B	Inductor (L)
C	Capacitance (C)
D	All of the above
--	
Marks	1.5
Unit	II

Id	116
Question	In shunt peaked amplifier Bandwidth enhancement is provided by
A	Resistance (R)
B	Inductor (L)
C	Capacitance (C)
D	All of the above
--	
Marks	1.5
Unit	II

Id	117
Question	As frequency, increases gain falls of because of
A	Resistance
B	Inductor loading
C	Capacitive loading
D	All of the above
--	
Marks	1.5
Unit	II

Id	118
Question	Gain of purely resistively loaded common source amplifier is proportional to....
A	$g_m * R_L$
B	$4 * g_m * R_L$
C	
D	R_L
--	
Marks	1.5
Unit	II


Id	119
Question	For shunt peaked amplifier bandwidth is Times larger than unpeaked ones.
A	1.2
B	1.72
C	5
D	10
--	
Marks	1.5
Unit	II


Id	120
Question	Phase distortion is objectionable for the
A	Bit errors
B	Gain
C	Both a and b
D	None
--	
Marks	1.5
Unit	II


Id	121
Question	Larger Bandwidth extension can be achieved by choosing larger
A	C
B	L
C	R
D	Both a and b
--	
Marks	1.5
Unit	III

Id	122
Question	Shunt peaking amplifier uses for bandwidth enhancer
A	Poles
B	Zeros
C	Both a and b
D	Conjugate poles
--	
Marks	1.5
Unit	III

Id	123
Question	The notion of cancelling pole with zero can be used to
A	Increase Bandwidth
B	Increase gain
C	Decrease bandwidth
D	None
--	
Marks	1.5
Unit	III

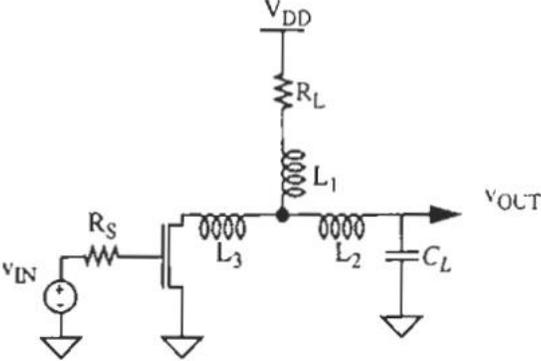Id	124
Question	<p>In the absence of L_1 the maximum bandwidth is times that of uncompensated case.</p> 
A	2
B	1.8
C	$\sqrt{2}$
D	1
--	
Marks	1.5
Unit	III

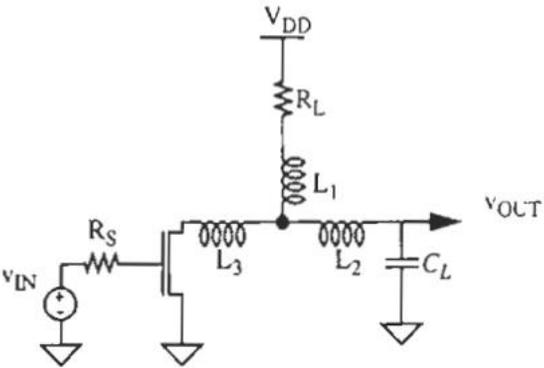Id	125
Question	<p>Risetime in the drain is improved by.....</p> 
A	L ₂
B	L ₃
C	C _L
D	R _L
--	
Marks	1.5
Unit	III

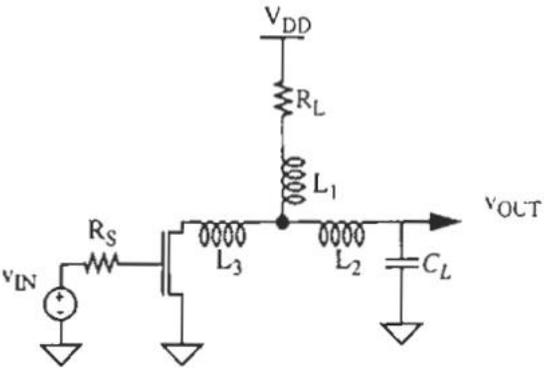
Id	126
Question	<p>In the diagram shown below network charges capacitance in</p>  <p>The diagram shows an electrical network. On the left, an input voltage source v_{IN} is connected in series with a resistor R_S. This series combination is connected to a node that branches into two paths: one through an inductor L_3 to ground, and another through an inductor L_1 to a node connected to a V_{DD} source through a resistor R_L. From this node, the circuit continues through an inductor L_2 to a final output node. This output node is connected to ground through a capacitor C_L and has an output voltage v_{OUT} indicated by an arrow pointing to the right.</p>
A	Series
B	Parallel
C	Both a and b
D	None
--	
Marks	1.5
Unit	III


Id	127
Question	In shunt and double-series peaking small bridging capacitance is added across the inductors to create
A	Series resonance
B	Parallel resonance
C	Connection
D	None
--	
Marks	1.5
Unit	III

Id	128
Question	In shunt and double-series peaking Couple inductances should each have a value
A	$L = \frac{R^2 C_L}{2(1 + k)}$
B	$L = \frac{R^2 C_L}{(1 + k)}$
C	$L = \frac{2 * R^2 C_L}{(1 + k)}$
D	$L = \frac{R^2 C_L}{(2 + k)}$
--	
Marks	1.5
Unit	III

Id	129
Question	In shunt and double-series peaking bridging capacitance should have a value of
A	$C_c = \frac{4 * C_L}{k} \left[\frac{1 - k}{1 + k} \right]$
B	$C_c = \frac{C_L}{4} \left[\frac{1 - k}{1 + k} \right]$
C	$C_c = \frac{C_L}{2} \left[\frac{1 - k}{1 + k} \right]$
D	$C_c = \frac{2 * C_L}{k} \left[\frac{1 - k}{1 + k} \right]$
--	
Marks	1.5
Unit	III

Id	130
Question	With T coil bandwidth enhancement technique we can get times bandwidth
A	1.414
B	2
C	1.5
D	2.83
--	
Marks	1.5
Unit	III

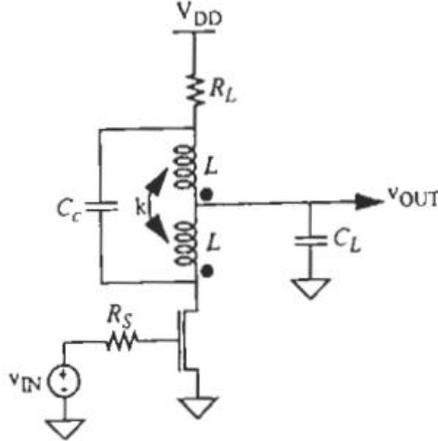Id	131
Question	<p>The following diagram shows bandwidth enhancement circuit method</p> 
A	T-coil bandwidth enhancement
B	Shunt and series peaking
C	Zero peaked
D	Shunt peaked
--	
Marks	1.5
Unit	III

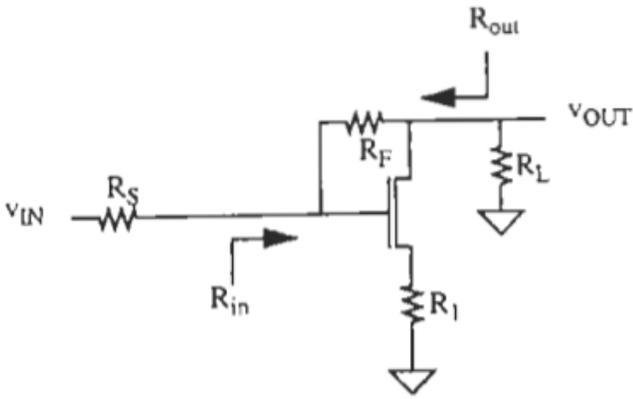Id	132
Question	<p>The following diagram shows</p> 
A	Series-shunt amplifier
B	Shunt-series amplifier
C	Shunt-shunt amplifier
D	Series-series amplifier
--	
Marks	1.5
Unit	III

Id	133
Question	In shunt series amplifier Voltage gain of the amplifier from the gate to drain is approximately
A	$\frac{R_F}{R_1}$
B	$-\frac{R_F}{R_1}$
C	$-\frac{R_L}{R_1}$
D	$\frac{R_L}{R_1}$
--	
Marks	1.5
Unit	III

Id	134
Question	In shunt series amplifier Voltage gain of the amplifier R_{in} is approximately given by
A	$R_{in} = \frac{R_F}{1 - \frac{R_L}{R_1}}$
B	$R_{in} = \frac{2 * R_F}{1 + \frac{R_L}{R_1}}$
C	$R_{in} = \frac{2 * R_F}{1 - \frac{R_L}{R_1}}$
D	$R_{in} = \frac{R_F}{1 + \frac{R_L}{R_1}}$
--	
Marks	1.5
Unit	III

Id	135
Question	Effective transconductance of a common-source amplifier with source degeneration is ...
A	$g_{m,\text{eff}} = \frac{2 * g_m}{1 + g_m R_1}$
B	$g_{m,\text{eff}} = \frac{g_m}{1 + g_m R_1}$
C	$g_{m,\text{eff}} = \frac{g_m}{1 - g_m R_1}$
D	$g_{m,\text{eff}} = \frac{2 * g_m}{1 - g_m R_1}$
--	
Marks	1.5
Unit	III

Id	136
Question	f_T doubling circuits it increases bandwidth upto...
A	50% increases
B	30% increases
C	80% increases
D	100% increases
--	
Marks	1.5
Unit	III

Id	137
Question	Gain over narrow frequency range centered about some high frequency is the characteristics of ...
A	Power amplifier
B	Broadband amplifier
C	Tuned amplifier
D	Ultra-wideband amplifier
--	
Marks	1.5
Unit	III

Id	138
Question	Ideally for amplifiers the gain bandwidth product must be
A	Greater than 1
B	Constant
C	Zero
D	Infinity
--	
Marks	1.5
Unit	III

Id	139
Question	At low frequencies inductor acts as
A	Short circuit
B	Open circuit
C	Zero reactance
D	Both a and c
--	
Marks	1.5
Unit	III

Id	140
Question	A tuned amplifier uses load
A	Resistive
B	Capacitive
C	LC tank
D	Inductive
--	
Marks	1.5
Unit	III

Id	141
Question	A tuned amplifier is generally operated in operation
A	Class A
B	Class C
C	Class B
D	None
--	
Marks	1.5
Unit	III

Id	142
Question	A tuned amplifier is used in applications
A	Radio frequency
B	Low frequency
C	Audio frequency
D	None
--	
Marks	1.5
Unit	III

Id	143
Question	At series or parallel resonance, the circuit power factor is
A	0
B	5
C	1
D	8
--	
Marks	1.5
Unit	III

Id	144
Question	The voltage gain of a tuned amplifier is at resonant frequency
A	Minimum
B	Maximum
C	Half-way between maximum and minimum
D	Zero
--	
Marks	1.5
Unit	III

Id	145
Question	At parallel resonance, the line current is
A	Minimum
B	Maximum
C	Infinity
D	Zero
--	
Marks	1.5
Unit	III

Id	146
Question	At series resonance, the circuit offers impedance
A	Zero
B	Maximum
C	Minimum
D	None
--	
Marks	1.5
Unit	III

Id	147
Question	A resonant circuit contains elements
A	R and L only
B	R and C only
C	C and L
D	Only R
--	
Marks	1.5
Unit	III

Id	148
Question	At series or parallel resonance, the circuit behaves as a load
A	Capacitive
B	Resistive
C	Inductive
D	None
--	
Marks	1.5
Unit	III

Id	149
Question	When either L or C is increased, the resonant frequency of LC circuit
A	Remains same
B	Increases
C	Decreases
D	Insufficient data
--	
Marks	1.5
Unit	III

Id	150
Question	The Q of an LC circuit is given by
A	$2\pi f_r * R$
B	$\frac{R}{2\pi f_r}$
C	$\frac{2\pi f_r L}{R}$
D	$\frac{R}{2\pi f_r L}$
--	
Marks	1.5
Unit	III

Id	151
Question	Compute the inductance associated with the leads of the high frequency capacitor of capacitance value 47pF at 1GHz whose dielectric medium consists of an aluminium oxide possessing a series loss tangent of 10^{-4} (assumed to be frequency independent) and whose leads are 1.25cm AWG 26 copper wires ($\sigma_{cu} = 64.516 * 10^6 \Omega^{-1}m^{-1}$)
A	24.38nH
B	24.38pH
C	24.38 μ H
D	24.38mH
--	
Marks	1.5
Unit	I

Id	152
Question	Compute the series resistance associated with the leads of the high frequency capacitor of capacitance value 47pF at 1GHz whose dielectric medium consists of an aluminium oxide possessing a series loss tangent of 10^{-4} (assumed to be frequency independent) and whose leads are 1.25cm AWG 26 copper wires ($\sigma_{cu} = 64.516 * 10^6 \Omega^{-1}m^{-1}$)
A	151.789m Ω
B	1.51789m Ω
C	15.1789m Ω
D	151.789 $\mu\Omega$
--	
Marks	1.5
Unit	I

Id	153
Question	Compute the parallel leakage resistance of the high frequency capacitor of capacitance value 47pF at 1GHz whose dielectric medium consists of an aluminium oxide possessing a series loss tangent of 10^{-4} (assumed to be frequency independent) and whose leads are 1.25cm AWG 26 copper wires ($\sigma_{cu} = 64.516 * 10^6 \Omega^{-1}m^{-1}$)
A	33.9 K Ω
B	3.39 K Ω
C	33.9 M Ω
D	339 K Ω
--	
Marks	1.5
Unit	I

Id	154
Question	Capacitance increases with _____
A	Increase in distance between the plates
B	Decrease in plate area
C	Decrease in distance between the plates
D	Increase in density of the material
--	
Marks	1.5
Unit	I

Id	155
Question	Typical sizes of surface mounted wire wound inductors range from
A	60 by 30 mils to 180 by 120 mils
B	200 by 240 mils to 300 by 280 mils
C	360 by 300 mils to 400 by 380 mils
D	420 by 440 mils to 500 by 480 mils
--	
Marks	1.5
Unit	I